

Chapter 11: Ohm's Law and Resistance

Ohm's Law

Ohm's Law describes the behaviour of most metallic conductors at constant temperature. You will remember it by the equation:

$$V = I \times R \quad \text{where:}$$


V is the voltage (also known as the **potential difference**) across the material in volts

I is the current in amps

R is the resistance in ohms (symbol Ω)

This can be rearranged to calculate the **resistance**:

$$R = \frac{V}{I}$$

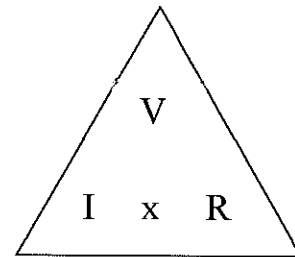

Example 1

A 47Ω resistor has a current of 0.65 A flowing through it. Calculate the potential difference across it.

Answer

$$\begin{aligned} V &= IR \\ &= 0.65 \times 47 \\ &= 31 \text{ V} \end{aligned}$$

Example 2

A $47 \text{ k}\Omega$ resistor is attached to a 3.0 V supply. Calculate the current.

Answer

$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{3.0}{47 \times 10^3} \\ &= 6.4 \times 10^{-5} \text{ A} \end{aligned}$$

Example 3


A 230 V supply is attached to a heater. A current of 1.2 A flows. Calculate its resistance.

Answer

$$\begin{aligned} R &= \frac{V}{I} \\ &= \frac{230}{1.2} \\ &= 190 \Omega \text{ (to 2 sig fig)} \end{aligned}$$

Questions

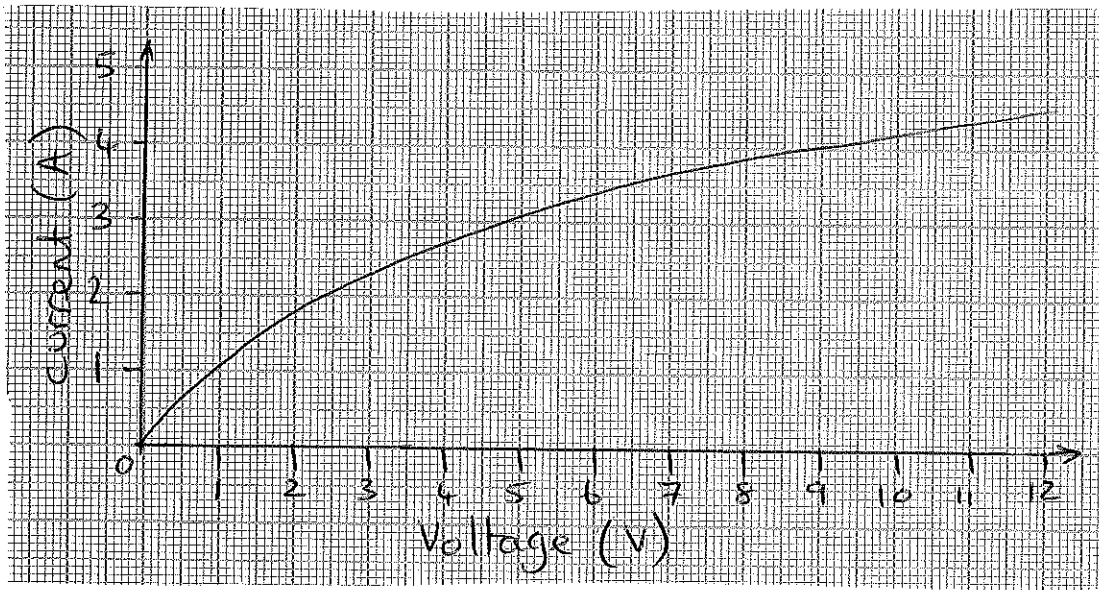1. Look at the graph below. It shows the relationship between voltage and current for a heater.



- a) Read off the values of current at a voltage of 6V and then calculate the resistance of the heater.
 - b) Repeat this process to calculate the resistance of the heater at $V=10V$
2. Voltmeters are designed to have high resistance so little current flows through them when placed in parallel across a component.

A voltmeter has a resistance of $450\text{ M}\Omega$. It can read voltages up to $200V$. At this voltage what current will flow through the meter?

3. A current of 2.8 mA flows through a $47\text{ M}\Omega$ resistor. Calculate the potential difference across the resistor in volts.
4. A resistor has a value of $150\text{ k}\Omega$ with a manufacturing tolerance of $\pm 5\%$. Calculate the maximum possible current when it is connected to a 1.50 V supply?